

10/20/23

ECE 2250; HW 5

Campbell, Brigham

Problem 3.30: Find v_1 & v_2

$$150\Omega \parallel 75\Omega = 50\Omega$$

$$90\Omega \parallel 90\Omega = 45\Omega$$

$$\frac{45\Omega}{45\Omega + 90\Omega} \cdot 3V = 1V$$

$$v_1 = 1V \cdot \frac{50\Omega}{50\Omega + 40\Omega} \approx \underline{\underline{0.556V}}$$

$$v_2 = 1V \cdot \frac{30\Omega}{30\Omega + 60\Omega} \approx \underline{\underline{0.333V}}$$

Problem 3.32: Find v_x

$$v_x = v_s - v_1$$

$$v_s = 45V \cdot \frac{20k\Omega}{25k\Omega}$$

$$= 36V$$

$$v_1 = 45V \cdot \frac{90k\Omega}{150k\Omega}$$

$$= 27V$$


$$v_x = \underline{\underline{9V}}$$

$$v_x = v_s \left(\frac{4}{5} - \frac{3}{5} \right) = v_s \frac{1}{5}$$

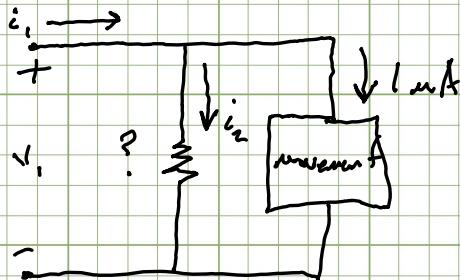Problem 3.33:

A short resistor and a 50mV , 1mA d'Arsonval movement are used to build an 5A ammeter.

A resistance of $20\text{m}\Omega$ is placed across the terminals of the ammeter. What's the new full-scale range?



$$i_1 = 5\text{A} \quad i_2 = 4999\text{ mA}$$

$$V_1 = 50\text{mV} \quad \frac{50\text{mV}}{4999\text{ mA}} \approx 10\text{m}\Omega$$

$$20\text{m}\Omega \parallel 10\text{m}\Omega = 6.67\text{m}\Omega$$

$$\text{Full-scale} = 1\text{mA} + \frac{50\text{mV}}{6.67\text{m}\Omega} = \underline{\underline{7.5\text{A}}}$$



Problem 3.37: Find R_v for each of the following full-scale readings: 50 V, 5 V, 250 mV, 25 mV

$$I_{mA} = \frac{(50V - 20mV)}{R_v} \Rightarrow R_v = \underline{\underline{49,980 \Omega}}$$

$$I_{mV} = \frac{(5V - 20mV)}{R_v} \Rightarrow R_v = \underline{\underline{4,980 \Omega}}$$

$$I_{mV} = \frac{(250mV - 20mV)}{R_v} \Rightarrow R_v = \underline{\underline{230 \Omega}}$$

$$I_{mV} = \frac{(25mV - 20mV)}{R_v} \Rightarrow R_v = \underline{\underline{5 \Omega}}$$

Problem 3.51: Bridge circuit has 21 V dc.

Bridge is balanced when $R_1 = 800 \Omega$

$$R_2 = 1200 \Omega$$

$$R_3 = 600 \Omega$$

a) what is R_x ?

b) How much current is supplied?

c) Which resistor absorbs the most power? How much?

d) Which absorbs the least? How much?

$$R_x = R_2 \cdot \frac{R_3}{R_1} = \underline{\underline{900 \Omega}}$$

$$\underline{\underline{21 V}}$$

$$R_{eq} = R_1 / R_2 + R_3 / R_x$$

$$\underline{\underline{R_{eq}}}$$

$$= 840 \Omega$$

$$= 25 \text{ mA}$$

$$V_x = 21 V \cdot \frac{R_x}{R_x + R_{eq}} = 9 V \rightarrow \text{Voltage over } R_x \text{ is } \underline{\underline{R_x}}$$

$$12 V \rightarrow V_o \text{ (voltage over } R_1 \text{ is } \underline{\underline{R_1}})$$

$$\frac{9 V^2}{600 \Omega} = 0.135 W$$



$$\frac{12 V^2}{800 \Omega} = 0.180 W$$

R_1 consumes the most at 180 mW

$$\frac{9V^2}{900\Omega} = 0.09W \quad \frac{12V^2}{1200\Omega} = 0.12W$$

R_x consumes the least at 90 mW

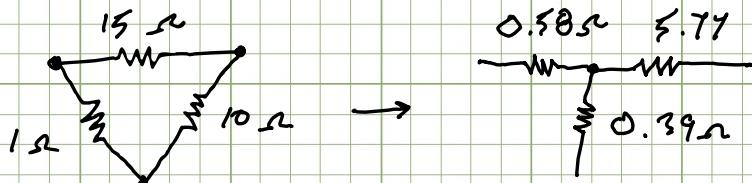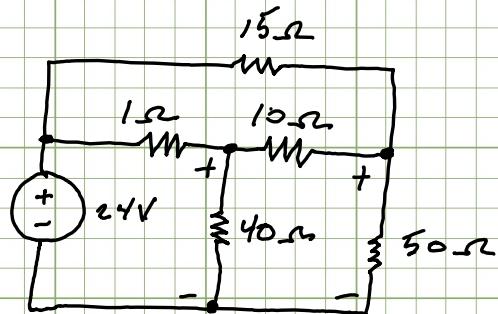Problem 3.58: Use a delta-wye transformation to find the voltages V_1 , $\not V_2$



$$\frac{15\Omega \cdot 10\Omega}{1\Omega + 10\Omega + 15\Omega} \approx 5.77\Omega$$

$$\frac{1\Omega \cdot 10\Omega}{1\Omega + 10\Omega + 15\Omega} \approx 0.39\Omega$$


$$\frac{1\Omega \cdot 15\Omega}{1\Omega + 10\Omega + 15\Omega} = 0.58\Omega$$

$$24V - 0.6V = 23.4V$$

$$v_1 = 23.18V$$

$$v_2 = 20.98V$$

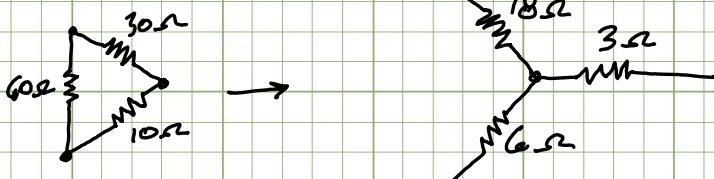
Problem 3.59: Find i_1 , i_2 , v , and the power supplied.



$$\frac{30\Omega \cdot 10\Omega}{100\Omega} = 3\Omega$$

$$\frac{30\Omega \cdot 6\Omega}{100\Omega} = 18\Omega$$
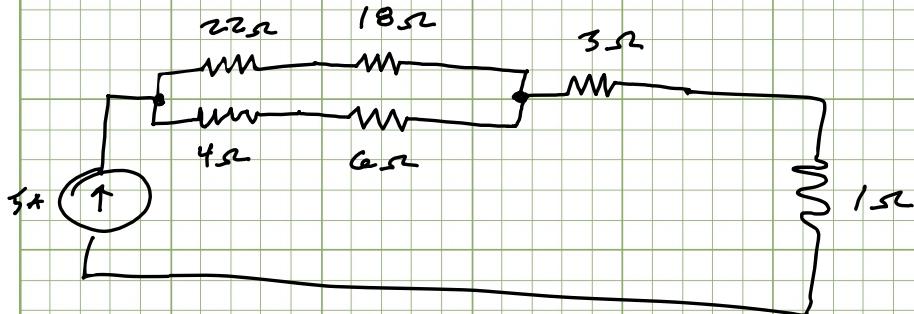
$$\frac{6\Omega \cdot 10\Omega}{100\Omega} = 6\Omega$$



$$12\Omega \quad \text{power} = \frac{60V^2}{12\Omega} = \underline{\underline{300W}}$$

$$60V \quad V = \underline{\underline{-6V}}$$

$$\frac{6V}{60\Omega} = 0.1A \quad i_1 = \underline{\underline{4A}} \quad i_2 = \underline{\underline{3.9A}}$$

Problem 3.60: Find i_o , if the power dissipated in the 140Ω resistor.

$$[([(8\Omega + 12\Omega) \parallel 60\Omega] + 20\Omega] \parallel 140\Omega] + 22\Omega$$

$$= 50\Omega$$



$$(50\Omega \parallel 75\Omega) + 10\Omega = 40\Omega$$

$$i_o = \frac{180V}{75\Omega} = \underline{\underline{2.4A}}$$

$$\frac{180V}{50\Omega} = 3.6A \quad 180V - 3.6A \cdot 22\Omega = 100.8V$$

$$\frac{100 \cdot 8V^2}{140\Omega} \approx 72.6W$$

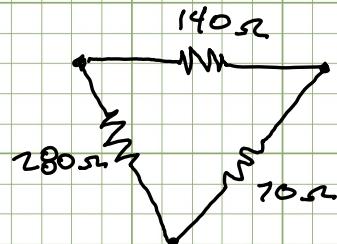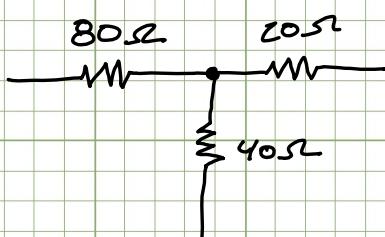
Problem 3.62: Find $i_0, i_1, i_2, ?$ the power delivered.



$$\frac{80\Omega \cdot 20\Omega + 20\Omega \cdot 40\Omega + 40\Omega \cdot 80\Omega}{40\Omega} = 140\Omega$$

$$\frac{1600\Omega^2}{20\Omega} = 280\Omega$$
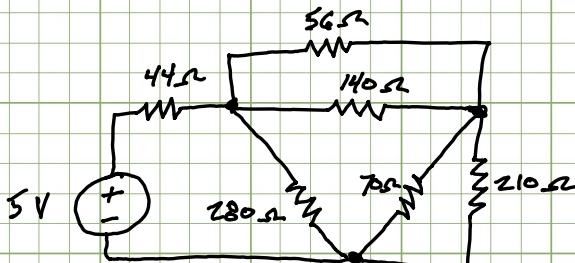
$$\frac{5600\Omega^2}{80\Omega} = 70\Omega$$



$$\left(\frac{70\Omega}{210\Omega} + \frac{56\Omega}{140\Omega} \right) / 280\Omega + 44\Omega \approx 113.5\Omega$$

$$\frac{5V^2}{113.5\Omega} \approx \underline{\underline{220\text{ mW}}}$$


$$\frac{5V}{113.5\Omega} \approx 44\text{ mA} \cdot \frac{280\Omega}{280\Omega + 92.5\Omega} \approx 33\text{ mA}$$


$$33\text{ mA} \cdot \frac{140\Omega}{140\Omega + 56\Omega} \approx \underline{\underline{23.6\text{ mA}}} = i_1$$

$$33\text{ mA} \cdot \frac{70\Omega}{210\Omega + 70\Omega} \approx \underline{\underline{8.25\text{ mA}}} = i_0$$

$$i_2 = 44\text{ mA} - i_0 = \underline{\underline{35.8\text{ mA}}} = i_2$$

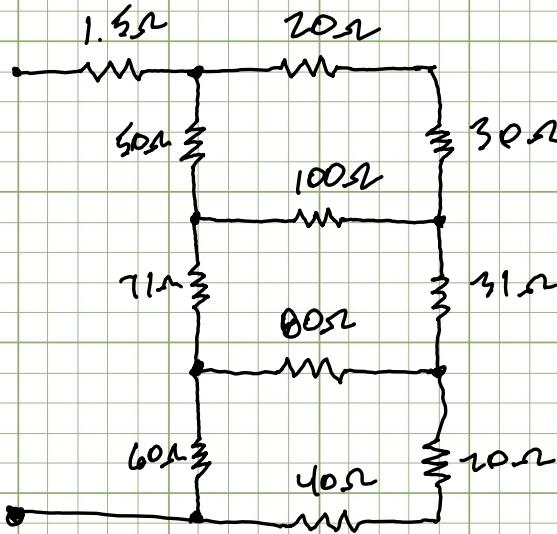Problem 3.63: Find the equivalent resistance.



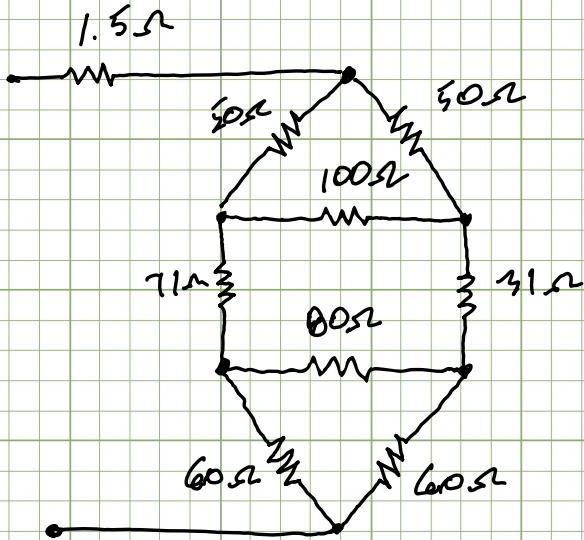



$$\frac{50\Omega \cdot 50\Omega}{200\Omega} = 12.5\Omega$$

$$\frac{100\Omega \cdot 50\Omega}{200\Omega} = 25\Omega$$

$$\frac{80\Omega \cdot 60\Omega}{200\Omega} = 24\Omega$$
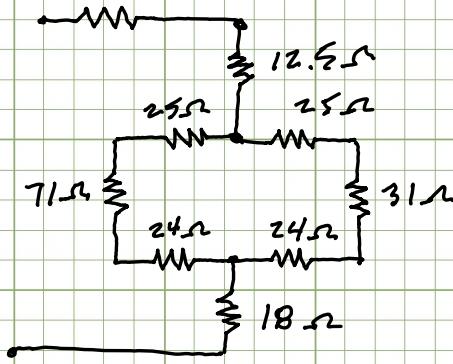
$$\frac{60\Omega^2}{200\Omega} = 18\Omega$$





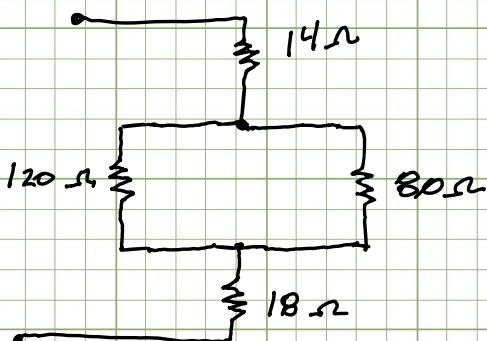

$$48\Omega + 18\Omega + 14\Omega = \underline{\underline{80\Omega}}$$

Problem 3.67: Use a γ - Δ transform to show that

$$R_{ab} = R_L : \text{f } R = R_L$$

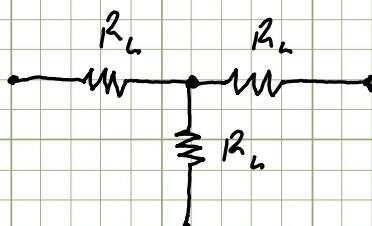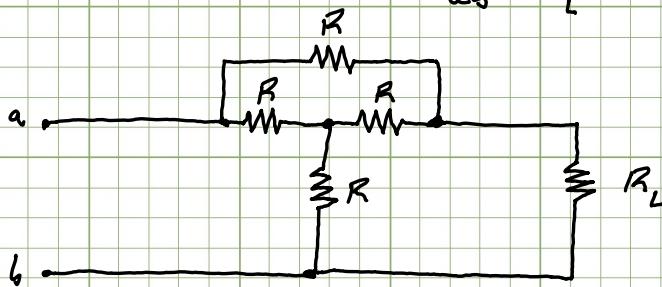

$$\frac{3R^2}{R} = 3R$$

